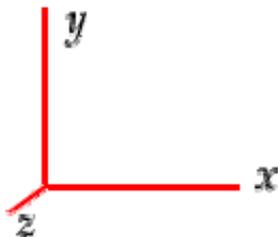


To specify directions, use the coordinate system shown below where  $+x$  is to the right,  $+y$  is toward the top of the page, and  $+z$  is out of the page.




Note the following terminology for directions:

- to the right ( $+x$ )
- to the left ( $-x$ )
- upward or toward the top of the page ( $+y$ )
- downward or toward the bottom of the page ( $-y$ )
- out of the page ( $+z$ )  $\odot$
- into the page ( $-z$ )  $\otimes$

### Section 1. Multiple Choice

1. Which of Kirchhoff's Laws is a result of Conservation of Mass (or alternatively Conservation of Charge)?
  - (a) Kirchhoff's Junction Law (also called Kirchhoff's Current Law or Current Rule)
  - (b) Kirchhoff's Loop Law (also called Kirchhoff's Voltage Law or Loop Rule)
  - (c) Neither of the above.
  - (d) Both of the above.
2. When an ion channel opens in a cell wall, monovalent (charge  $+e$ ) ions flow through the channel at a rate of  $2.7 \times 10^7$  ions/s. What is the current through the channel?
  - (a)  $2.7 \times 10^7$  A
  - (b)  $5.93 \times 10^{-27}$  A
  - (c)  $1.69 \times 10^{-12}$  A
  - (d)  $5.93 \times 10^{-13}$  A
  - (e)  $4.32 \times 10^{-12}$  A

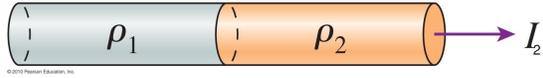Questions 3–4: Two wires of the same length and diameter are connected together in series as shown below.  $\rho_1 = \frac{1}{2}\rho_2$ . The current through wire 2 is  $I_2$ .



3. Compare the resistance of each wire.

- (a)  $R_1 = R_2$
- (b)  $R_1 = 2R_2$
- (c)  $R_1 = 4R_2$
- (d)  $R_1 = \frac{1}{2}R_2$
- (e)  $R_1 = \frac{1}{4}R_2$


4. Compare the current in each wire.

- (a)  $I_1 = I_2$
- (b)  $I_1 = \frac{1}{2}I_2$
- (c)  $I_1 = 2I_2$
- (d)  $I_1 = \frac{1}{4}I_2$
- (e)  $I_1 = 4I_2$

5. A metal wire of resistance  $R$  is cut into two pieces of equal length. The two pieces of wire are then connected together side by side, in parallel. What is the resistance of the two connected wires?


- (a)  $R/4$
- (b)  $R/2$
- (c)  $R$
- (d)  $2R$
- (e)  $4R$

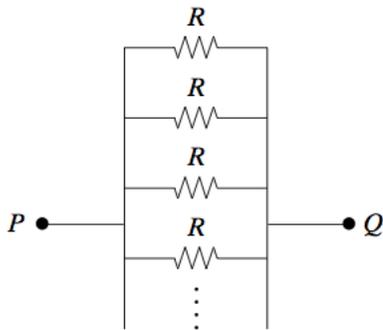6. As more identical resistors  $R$  are added to the parallel circuit shown here, the total resistance between points  $P$  and  $Q$



- (a) increases.
- (b) decreases.
- (c) remains the same.

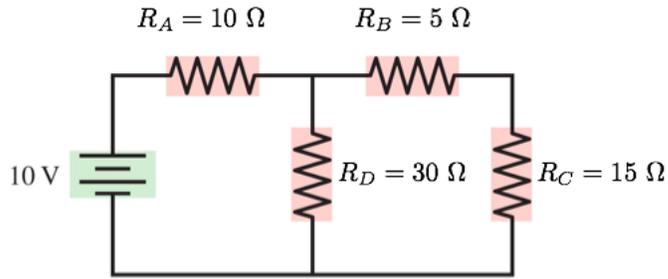Questions 7–9: Consider the circuit shown below.



7. What is the equivalent resistance of the resistors?

- (a)  $8.3 \Omega$
- (b)  $12 \Omega$
- (c)  $60 \Omega$
- (d)  $28 \Omega$
- (e)  $22 \Omega$


8. What is the current through the battery?

- (a)  $1.0 \text{ A}$
- (b)  $0.067 \text{ A}$
- (c)  $0.33 \text{ A}$
- (d)  $0.45 \text{ A}$
- (e)  $0.83 \text{ A}$

9. What is the current through resistor D?


- (a)  $0.33 \text{ A}$
- (b)  $0.15 \text{ A}$
- (c)  $0.18 \text{ A}$
- (d)  $0.20 \text{ A}$
- (e)  $0.27 \text{ A}$

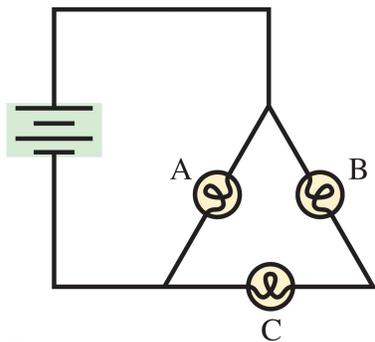Questions 10–13: Consider the circuit shown below. Assume that the light bulbs are identical. Note that you may find it better to redraw the circuit in a more conventional fashion.




10. Which individual bulbs are connected in parallel (with each other)?
- A and B
  - B and C
  - A and C
  - All three bulbs are connected in parallel with each other.
  - None of the bulbs are connected in parallel.
11. Which individual bulbs are connected in series (with each other)?
- A and B
  - B and C
  - A and C
  - All three bulbs are connected in parallel.
  - None of the bulbs are connected in parallel.
12. Rank the bulbs from brightest to dimmest.
- $B=C>A$
  - $B>C>A$
  - $B>C=A$
  - $A>B>C$
  - $A>B=C$
13. If you unscrew bulb B and remove it from its socket, what happens to the brightness of bulb A?
- It increases.
  - It decreases.
  - It remains the same.

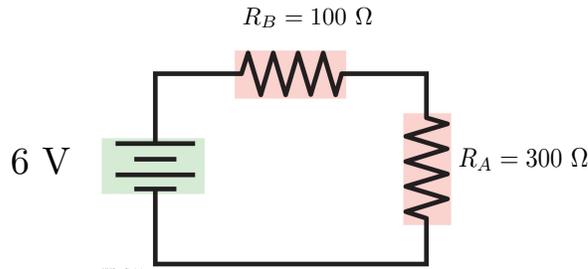14. What is the voltage across the  $300\ \Omega$  resistor?





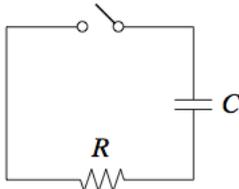- (a) 1.5 V
  - (b) 2.0 V
  - (c) 4.0 V
  - (d) 4.5 V
  - (e) 6.0 V
15. A resistor and an initially uncharged capacitor are connected in series to a battery, which is connected at  $t = 0$ . The current in the circuit
- (a) is constant because the emf supplied by the battery is constant.
  - (b) increases exponentially in time.
  - (c) initially increases and then levels off to a constant value.
  - (d) decreases exponentially in time.
  - (e) There is no current because the electrons cannot flow through the gap in the capacitor.
16. A simple circuit consists of a resistor  $R = 1200\ \Omega$  and a capacitor  $C = 1\ \text{mF}$ . The capacitor is initially charged to a potential of 3 V when a switch, that is initially open, is closed. At what time is the voltage across the capacitor 2 V?




- (a) 1.2 s
  - (b) 0.80 s
  - (c) 0.49 s
  - (d) 0.40 s
  - (e) 0.37 s
17. If you repeat the experiment exactly as before except with a resistor  $R = 600\ \Omega$ , then the capacitor will discharge
- (a) faster than before (i.e. less time).
  - (b) slower than before (i.e. more time).
  - (c) in the same time as before.

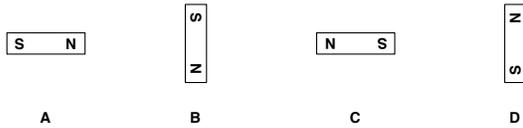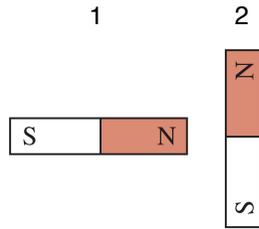18. Suppose that each magnet can spin about an axis through its center (but otherwise cannot move). You hold magnet 2 with your hand so that it cannot rotate. You then release magnet 1 from rest. Eventually it stops rotating and is at equilibrium. What will be the orientation of magnet 1?




- (a) A  
 (b) B  
 (c) C  
 (d) D

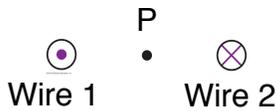19. Two wires carry equal and opposite currents, out of the page and into the page, as shown below. At point P, the net magnetic field is



- (a) in the  $+y$  direction.  
 (b) in the  $-y$  direction.  
 (c) in the  $+z$  direction.  
 (d) in the  $-z$  direction.  
 (e) zero.

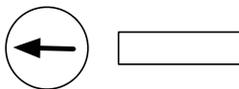
20. A compass and bar magnet are shown below. Use the compass to label the poles of the bar magnet.




Which image below shows the correct labels for the bar magnet?

- (a)   
 (b) 

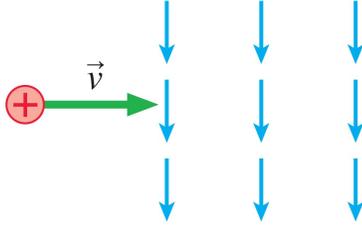21. When the positively charged ion below first enters the region of uniform magnetic field shown by the set of arrows, the magnetic force on the ion is:




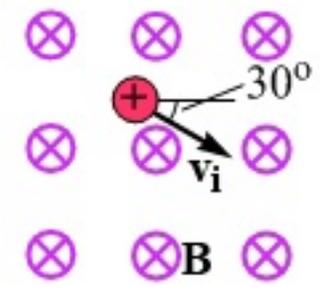- (a) in the  $+y$  direction.  
 (b) in the  $-y$  direction.  
 (c) in the  $+z$  direction.  
 (d) in the  $-z$  direction.  
 (e) zero.
22. The particle in the figure below has a charge of  $3.00 \times 10^{-6}$  C and a speed of  $2.00 \times 10^3$  m/s. It is in a uniform magnetic field, directed into the page, of  $5.00 \times 10^{-2}$  T. As the figure shows, the initial velocity of the particle is directed at  $30^\circ$  below the positive x-axis. What is the magnitude of the magnetic force acting on the particle?




- (a)  $1.5 \times 10^{-4}$  T  
 (b)  $2.6 \times 10^{-4}$  T  
 (c)  $3 \times 10^{-4}$  T  
 (d) 0.12 T  
 (e) zero

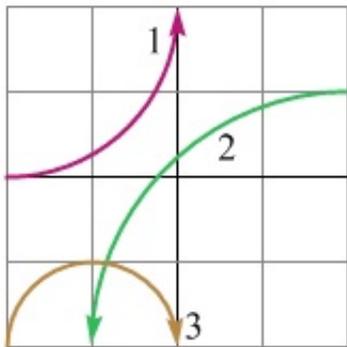Questions 23–24: The figure below shows the paths followed by three charged particles through a region of uniform magnetic field that is directed perpendicular to the page. All three particles are ions with charge  $+e$  or  $-e$ . Particle 2 has a positive charge.



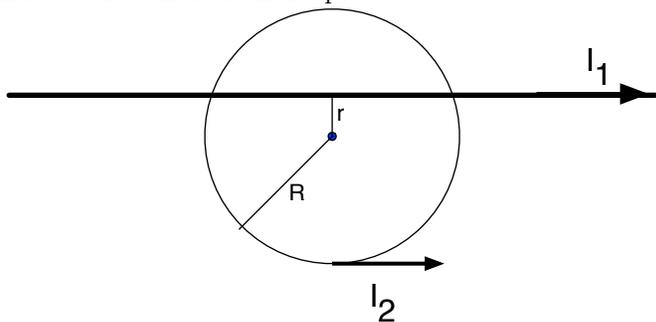23. In what direction is the magnetic field in the region?
- $+z$  direction
  - $-z$  direction
24. Which particle has the *least* mass?
- particle 1
  - particle 2
  - particle 3
25. A long wire crosses the face of a wire loop as shown below. The loop carries a current of 2 A counter-clockwise. The long wire carries a current of 1 A to the right. The long wire is  $r = 0.01$  m from the center of the loop, and the loop has a radius  $R = 0.03$  m. What is the magnitude of the net magnetic field at the center of the loop?



- $6.4 \times 10^{-5}$  T
- $2.0 \times 10^{-5}$  T
- $4.2 \times 10^{-5}$  T
- $6.2 \times 10^{-5}$  T
- $2.2 \times 10^{-5}$  T